

Symmetric square wave generator (or) Astable multivibrator:-

The ckt represents a square wave generator

Some part of output signal is feedback to positive terminal of op-amp i.e. βV_0 .

where V_0 - is output voltage.

β - feedback factor.

where β can be calculated by applying superposition theorem.

$$\beta = \frac{R_2}{R_1 + R_2}$$

$$V_{ref} = \beta V_0 = \frac{R_2}{R_1 + R_2} V_0$$

V_{ref} varies in between $+V_{sat}$ to $-V_{sat}$.

The feedback is also feedback to negative terminal through RC low pass combination.

Without any apply of input we are getting output so, it is called free running Oscillator.

Whenever feedback voltage (V_{fed}) is greater than V_{ref} i.e., $V_{fed} > V_{ref}$ switching takes place (f.e., $+V_{sat} \rightarrow -V_{sat}$ (or) $-V_{sat} \rightarrow +V_{sat}$).

Initially, assume

if

$$V_0 = +V_{sat} \Rightarrow V_{ref} = \beta V_{sat}$$

capacitor gets charges upto

$+V_{sat}$

when $\beta V_{sat} < V_{sat}$

$$\therefore V_c > V_{ref}$$

(switching takes place)

$$V_0 = -V_{sat}$$

$$\text{if } V_{ref} = -\beta V_{sat}$$

$$V_0 = -V_{sat}$$


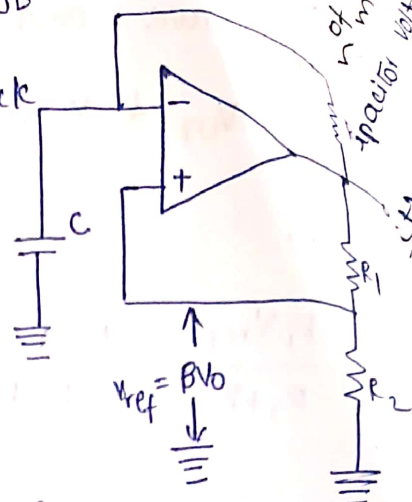


fig:- Astable multivibrator.

Both the states are Quasi States.

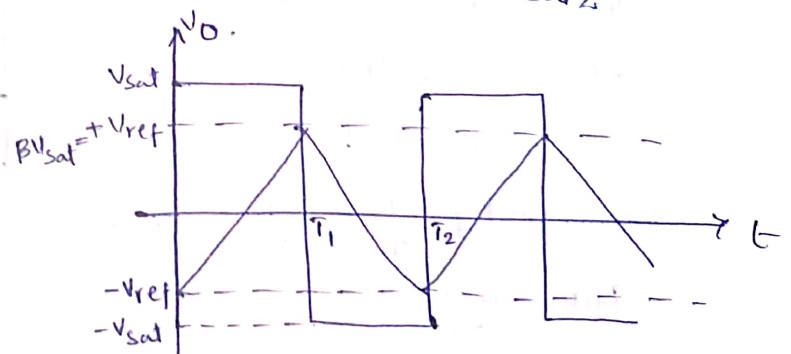

of sq. wave generator
Capacitor voltage is given as

$$V_c(t) = V_{\text{final}} + (V_{\text{initial}} - V_{\text{final}}) e^{-t/RC}$$

$$V_{\text{final}} = +V_{\text{sat}}$$

$$V_{\text{initial}} = -\beta V_{\text{sat}}$$

$$\begin{aligned} V_c(t) &= V_{\text{sat}} + (-\beta V_{\text{sat}} - V_{\text{sat}}) e^{-t/RC} \\ &= V_{\text{sat}} - V_{\text{sat}}(1+\beta) e^{-t/RC} \end{aligned}$$

$$V_c(t) = V_{\text{sat}}(1 - (1+\beta) e^{-t/RC})$$

at time $t=T_1$ the capacitor charges to $+\beta V_{\text{sat}}$.

$$V_c(T_1) = \beta V_{\text{sat}} = V_{\text{sat}}(1 - (1+\beta) e^{-T_1/RC})$$

$$1-\beta = (1+\beta) e^{-T_1/RC}$$

$$e^{+T_1/RC} = \frac{1+\beta}{1-\beta}$$

$$T_1 = RC \ln \left(\frac{1+\beta}{1-\beta} \right)$$

$$\text{Total Time period } T = 2RC \ln \left(\frac{1+\beta}{1-\beta} \right) \quad (\because \text{symmetric square wave})$$

$$\beta = \frac{R_2}{R_1 + R_2} = \frac{1}{2} = 0.5 \quad (\because R_1 = R_2)$$

$$T = 2RC \ln \left(\frac{1.5}{0.5} \right)$$

$$T = 2RC \ln 3$$

if $R_1 = 1.17 R_2$ then

$$T = 2RC$$

$$f_0 = \frac{1}{2RC}$$

$$V_0 = +V_{\text{sat}} \text{ to } -V_{\text{sat}}$$

$$V_0 = 2V_{\text{sat}}$$