
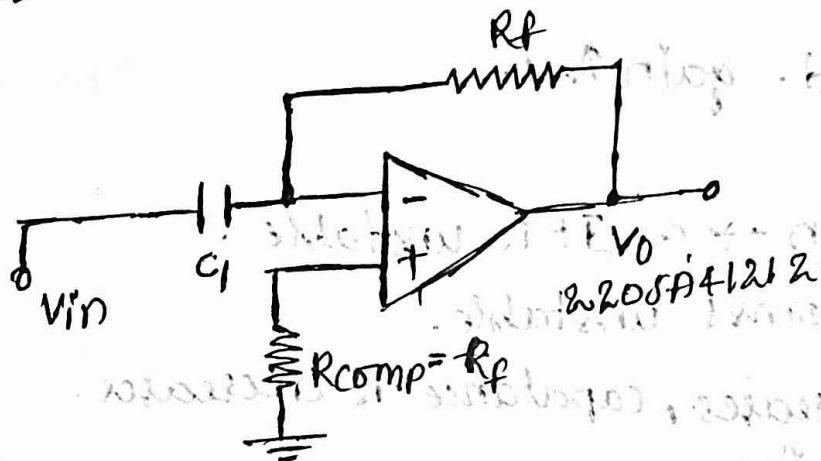


Differentiator:

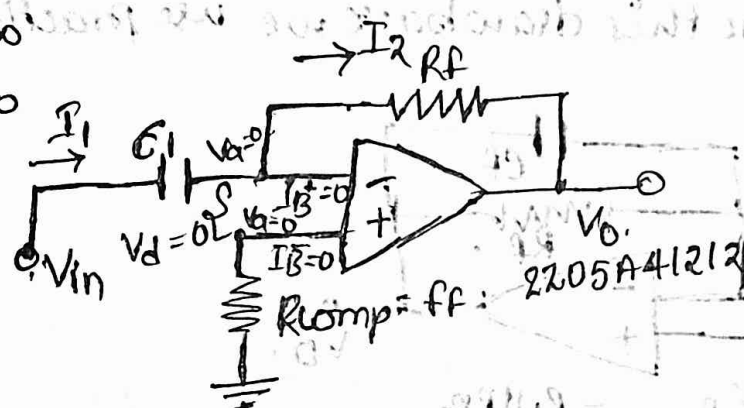

$$R_i = \infty$$

$$A = \infty$$



$$I_1 = I_2 + I_B$$

$$C_1 \frac{d(V_{in} - V_a)}{dt} = \frac{V_a - V_o}{R_f} + 0$$

$$V_o = -R_f C_1 \frac{dV_{in}}{dt}$$

$$V_o(s) = -R_f C_1 \cdot s V_{in}(s)$$

$$\frac{V_o(s)}{V_{in}(s)} = -s R_f C_1$$

$$\left| \frac{V_o(s)}{V_{in}(s)} \right| = +j\omega R_f C_1$$

$$\left| \frac{V_o(s)}{V_{in}(s)} \right| = A = |-j\omega R_f C_1|$$

$$|A| = \omega R_f C_1$$

$$|A| = 2\pi f R_f C_1$$

$$|A| = \frac{f}{f_a}$$


where $f_a = \frac{1}{2\pi R_f C_1}$ cut off frequency.

(i) If f is increased. gain \uparrow ed.

Drawback.

- as f is \uparrow ed. gain $\rightarrow \infty$. It is unstable. The system becomes unstable.
- as frequency increases, capacitance is decreases. $R_i = \infty$ is decreasing.

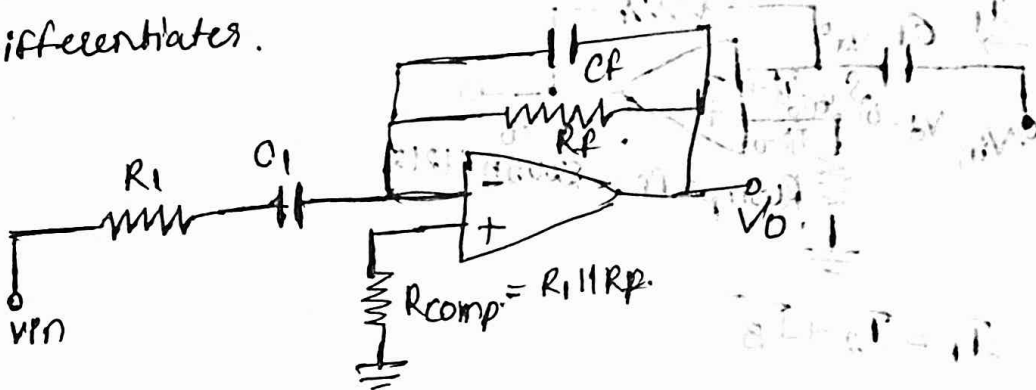
In order to overcome this drawback we use practical Differentiator.



$$R_i = \infty; A = \infty$$

$$R_1 + \frac{1}{C_1} = Z_1$$

$$R_f || C_f = \frac{R_f \times \frac{1}{C_f}}{R_f + \frac{1}{C_f}} = \frac{R_f}{1 + R_f C_f s} = Z_2$$

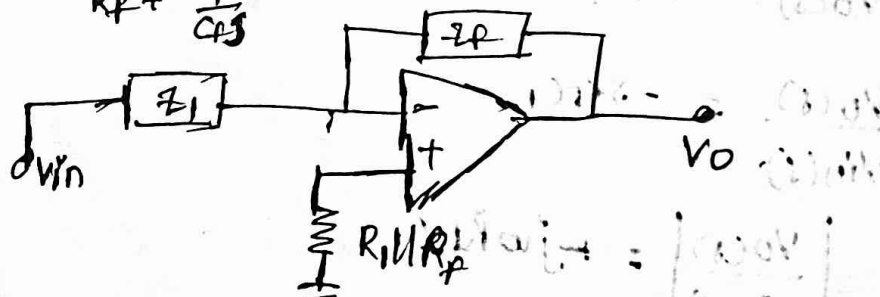

$$V_o = -\frac{Z_2}{Z_1} V_{in} = A = \begin{vmatrix} 0.00V \\ 0.00V \end{vmatrix}$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{-R_f}{1 + R_f C_f s} \cdot \frac{1}{R_i + \frac{1}{C_i s}}$$

$$= \frac{-R_f \cdot C_i s}{(1 + R_i C_i s)(1 + R_f C_f s)}$$

Let, $R_i C_i = R_f C_f$.

$$\frac{V_o(s)}{V_{in}(s)} = \frac{-R_f C_i s}{(1 + R_i C_i s)^2} = \frac{-R_f C_i s}{(1 + s/f_b)^2}$$

where $f_b = \frac{1}{2\pi R_i C_i}$

• problem:

the .

Design op-amp differentiator that will differentiate.

- (i) The input signal with max frequency of 100 Hz.
- (ii) Draw the output wave form for a sine wave of 1 volt peak to peak at 100 Hz is applied to differentiator.
- (iii) Repeat the above 2 for a square wave input.

Condition for design procedure.

- (i) a good differentiator may be designed if for the

following step

- (i) choose f_a = highest value of given input signal and assume the practical value of C_i is less than 1 micro Farad. 1 μ F

- (ii) choose $f_b = 10 f_a$ & assume $R_i C_i = R_f C_f$