

## Comparator:-

The Comparator is one of the non-linear application of operational amplifier.

A comparator is a circuit which compares a signal voltage applied at one input of an Op-amp with a known reference voltage at the other input. It is basically an open-loop Op-amp with output  $\pm V_{sat} (\approx V_{cc})$ .

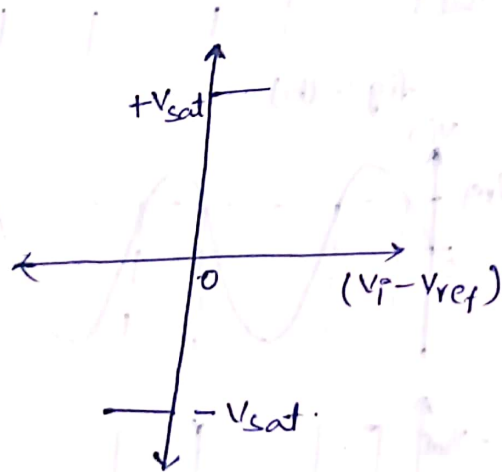


fig (a)

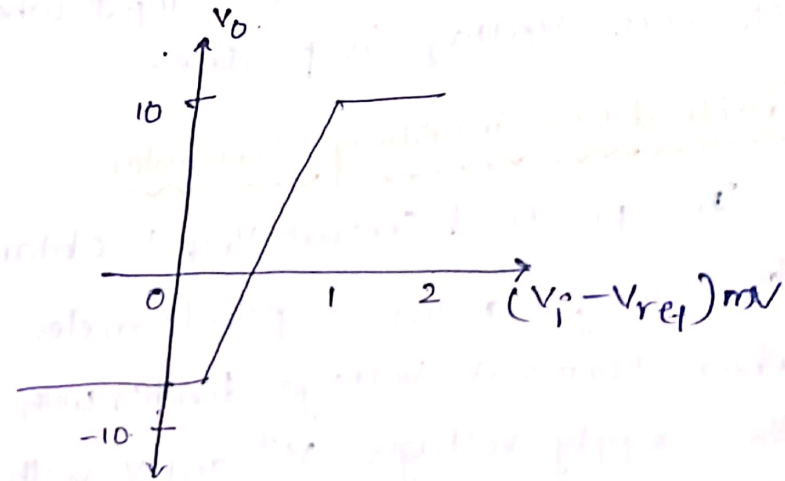


fig (b)

### Transfer characteristics

(a) Ideal Comparator

(b) Practical Comparator


- if input voltage  $V_i < V_{ref}$  then output is  $-V_{sat}$ .
- if input voltage  $V_i > V_{ref}$  then output is  $+V_{sat}$ .
- if input voltage  $V_i = V_{ref}$  then o/p is '0'.

Types of comparators:-

- (i) Non-inverting comparator
- (ii) Inverting comparator.

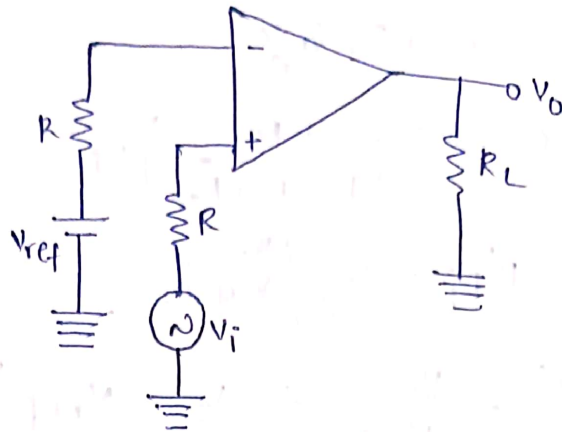(i) Non-inverting Comparator:-

The circuit represents a Non-inverting Comparator in which reference voltage is connected across inverting terminal and input voltage at non-inverting terminal.



if  $V_i < V_{ref}$  so we get  $V_o = -V_{sat}$ .

$V_i > V_{ref}$   $V_o = +V_{sat}$ .

fig(b) represents an output waveform for a sinusoidal input when reference voltage is negative. fig(c) represents an input and output waveform for a sine wave input when reference voltage is positive.



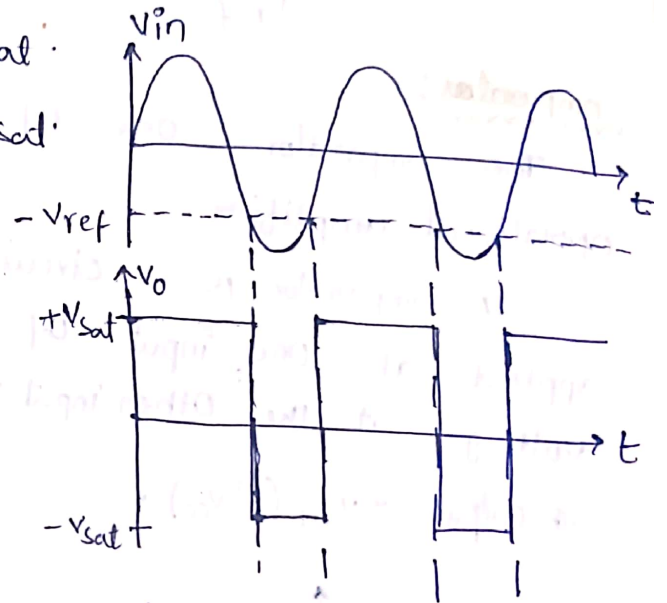


fig :- (b)

Practical non-inverting Comparator:-

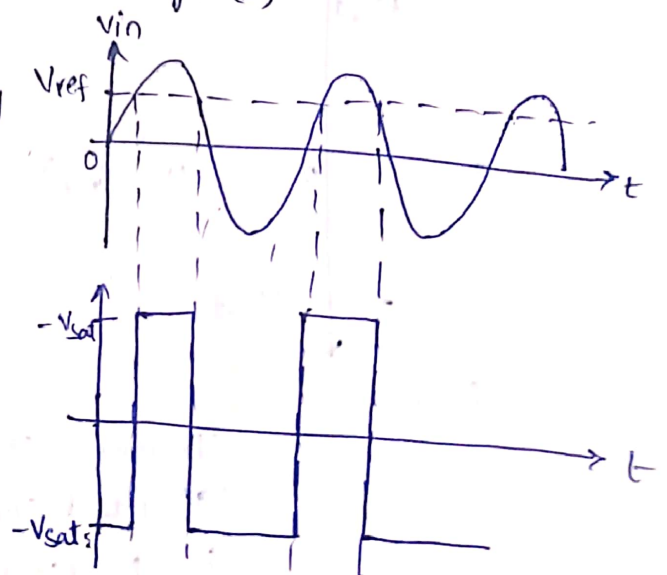In practical circuit  $V_{ref}$  is obtained by using a  $10k\Omega$  potentiometer which forms a voltage divider with the supply voltages  $V^+$  and  $V^-$  with the wiper connected to (-) input terminal. Thus  $V_{ref}$  of desired amplitude and polarity can be obtained by simply adjusting the  $10k\Omega$  potentiometer.



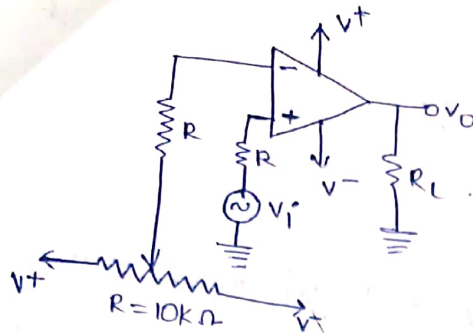

### Inverting comparator:-

The circuit represents an inverting comparator in which input is connected at inverting terminal and reference voltage at non-inverting terminal.

When  $V_i < V_{ref}$  then  $V_o = +V_{sat}$   
 When  $V_i > V_{ref}$  then  $V_o = -V_{sat}$



fig(b) represents the i/p & o/p waveforms when known reference voltage is positive.

### Practical Inverting comparator:-


In practical circuit  $V_{ref}$  is obtained by using a  $10k\Omega$  potentiometer which forms a voltage divider with the

supply voltages  $V^+$  and  $V^-$  with the wiper connected to (+) input terminal.

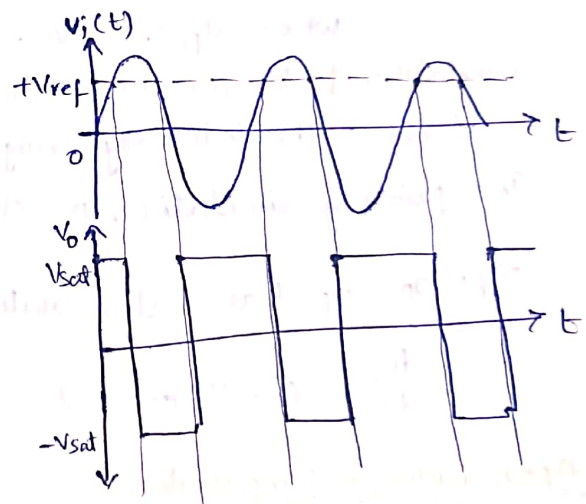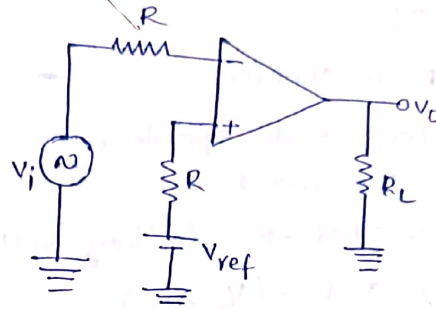Thus a desired amplitude and polarity of  $V_{ref}$  can be obtained by adjusting  $10k\Omega$  potentiometer.




fig(b)

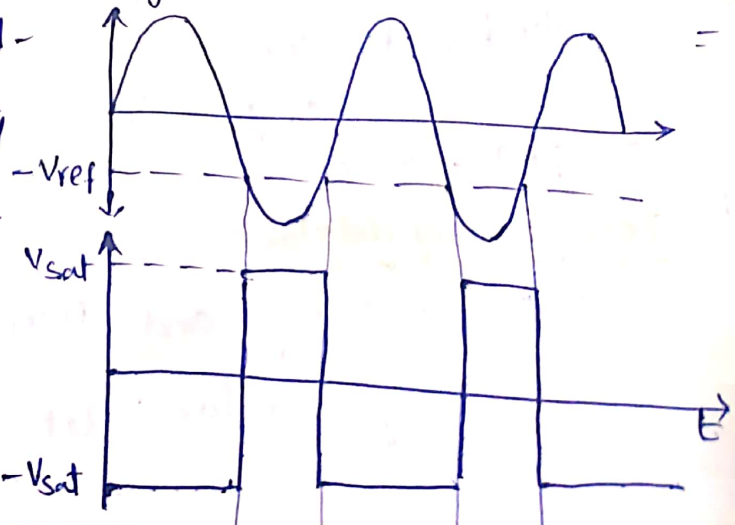






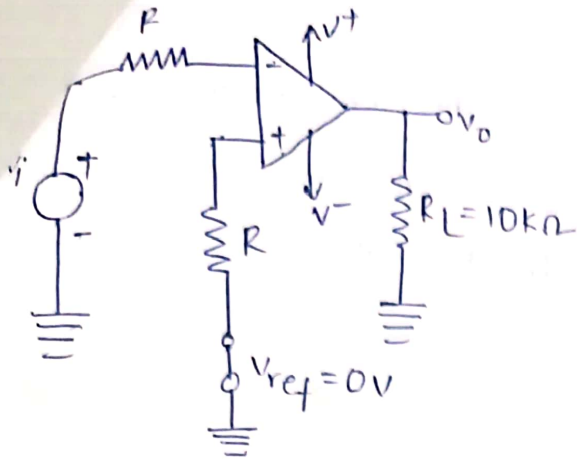provided that  $V_{ref}$  is set to zero. The output is shown is also known as "sine to square wave generator".





Zero - Crossing detector

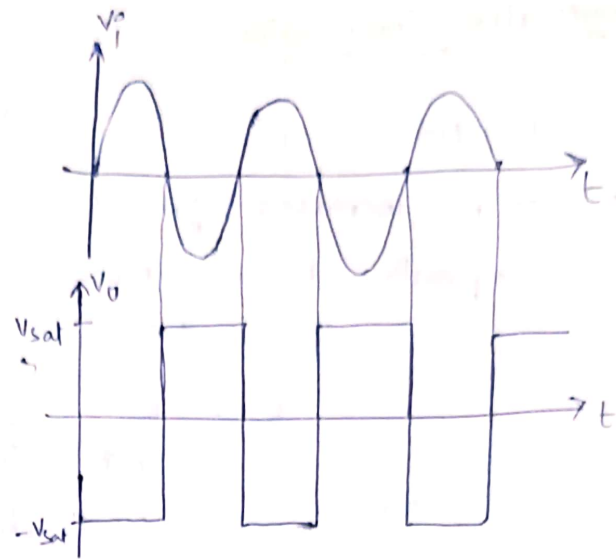
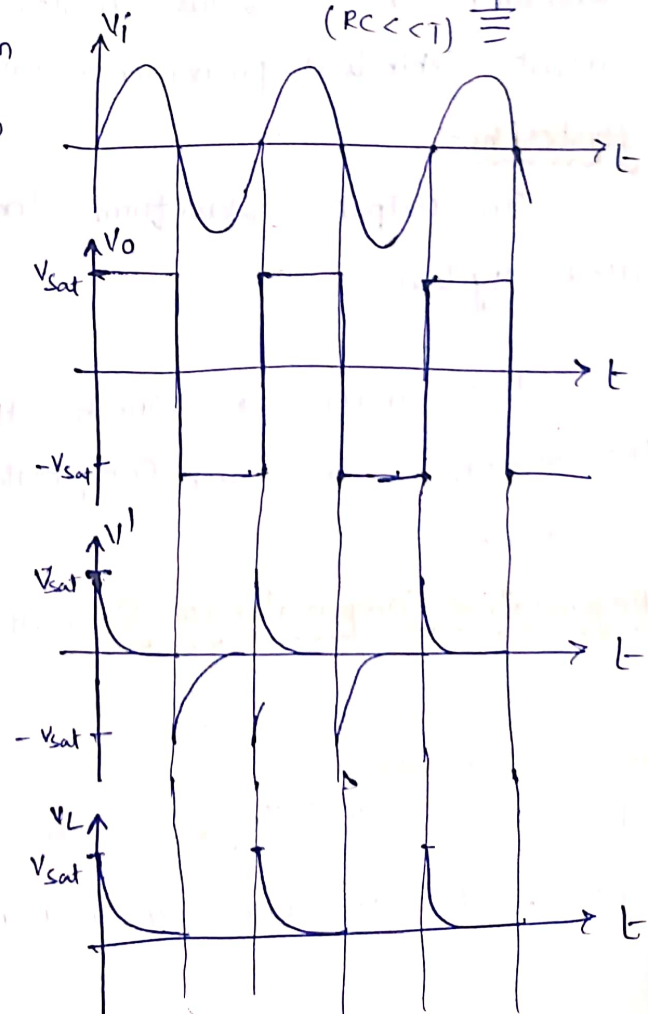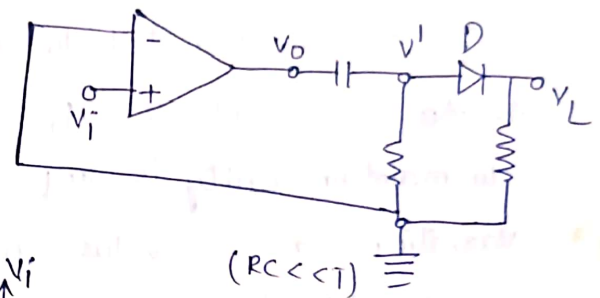
### Time marker generator:-

The circuit represents a time marker generator. The output of Zero Crossing detector is differentiated by RC Circuit. So, that  $V'$  is series of positive and negative pulses. The negative portion is clipped when it passed through a Diode D and the output waveform  $V_L$  is shown.



So, with the help of this ckt Sinusoid has been converted into a train of positive pulses of Spacing T which may used for triggering the monoshots, SCR, Sweep Voltage of CRT etc.

### Phase detector:-

The phase angle between two Voltages can also be measured using the time marker generator.

The time interval is proportional to the phase difference. measure phase angles from 0 to 360° with such a circuit.

### Regenerative Comparator

if positive feedback is added to the comparator circuit, gain can be increased greatly. Consequently, the transfer curve of comparator becomes more close to ideal curve.

$$V_o = -A_{OL} V_i$$

$$V_i = \frac{V_o}{-A_{OL}} \Rightarrow V_i \downarrow$$


then it is similar to ideal characteristics.

$$\text{closed loop gain } A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta} = \frac{-A_{OL}}{1 - (-A_{OL}\beta)}$$

$-A_{OL}\beta$  is adjusted to unity, then the gain with feedback,  $A_{CL}$  becomes infinite. Practically circuits, loop gain exactly to maintain unity is impossible due to supply voltage & temperature variations. So, a value greater than unity is chosen. then the circuit exhibits a phenomenon called hysteresis.
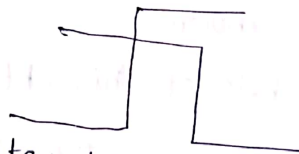
### Hysteresis:-


In output waveform, some discontinuous exists it is called Hysteresis.



The circuit in which Hysteresis exists such comparators are known as Regenerative Comparators.
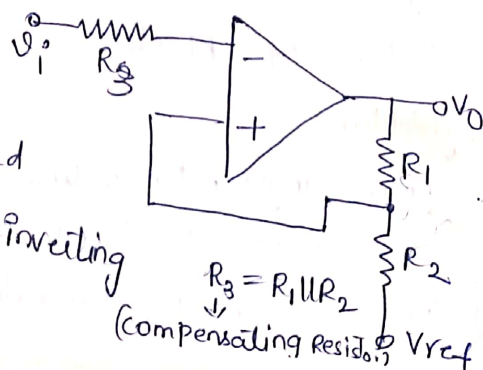
### Regenerative Comparator (or) Schmitt trigger:-

The figure shows a regenerative comparator in which input is applied at inverting terminal and feedback is connected to non-inverting





voltage  $V_i$  triggers the o/p  $V_o$  everytime it exceeds  
 range levels. Those voltage levels are known as  
 threshold voltage ( $V_{UT}$ ) & lower threshold voltage ( $V_{LT}$ ).  
 Hysteresis width:- The difference between these two threshold voltages  
 i.e.,  $V_{UT} - V_{LT}$

(38)

Suppose output  $V_o = +V_{sat}$

The voltage at (+) input terminal can be obtained by  
 using superposition theorem.

$$V_{UT} = \frac{V_{ref} R_1}{(R_1 + R_2)} + \frac{R_2 V_{sat}}{(R_1 + R_2)} \quad (\text{This voltage is upper threshold } V_{UT})$$

As long as  $V_i$  is less than  $V_{UT}$ , the output  $V_o$  remains constant  
 at  $+V_{sat}$ . When,  $V_i$  greater than  $+V_{UT}$ , the o/p regeneratively  
 switches to  $-V_{sat}$  and remains at this level as long as  $V_i > V_{UT}$ .


for  $V_o = -V_{sat}$  the voltage at (+) input terminal is

$$V_{LT} = \frac{V_{ref} R_1}{R_1 + R_2} - \frac{R_2 V_{sat}}{R_1 + R_2}$$

$$V_i > V_{LT} \Rightarrow -V_{sat}$$


$$V_i < V_{LT} \Rightarrow +V_{sat}$$

$$V_H = V_{UT} - V_{LT}$$

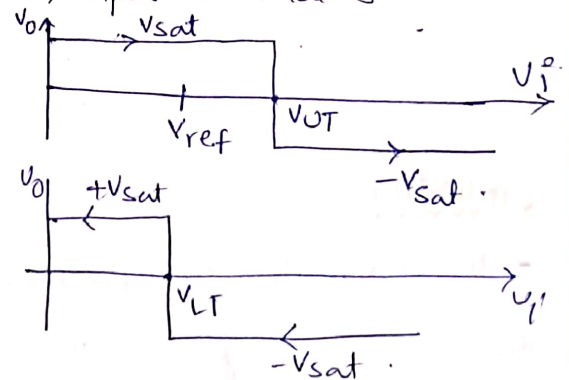

$$V_H = \frac{V_{ref} R_1}{(R_1 + R_2)} + \frac{R_2 V_{sat}}{R_1 + R_2} - \frac{V_{ref} R_1}{R_1 + R_2} + \frac{R_2 V_{sat}}{R_1 + R_2}$$

$$V_H = \frac{2R_2 V_{sat}}{R_1 + R_2}$$

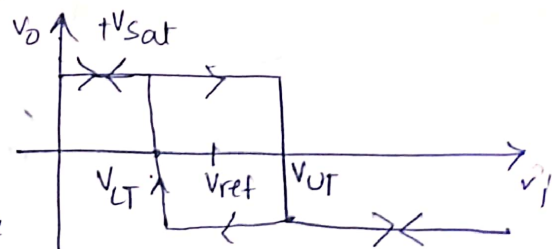

> Hysteresis circuit triggers output voltage  
 to the high volt for ~~Increasing~~ Increasing signals than for  
 decreasing ones


→ if peak to peak input voltage less than  $V_H$  then o/p is

Suppose Consider sinusoidal signal:-

if  $V_i < V_{UT}$  then  $V_o = +V_{sat}$

if  $V_i > V_{LT}$  then  $V_o = -V_{sat}$

We obtain an unsymmetrical square wave.

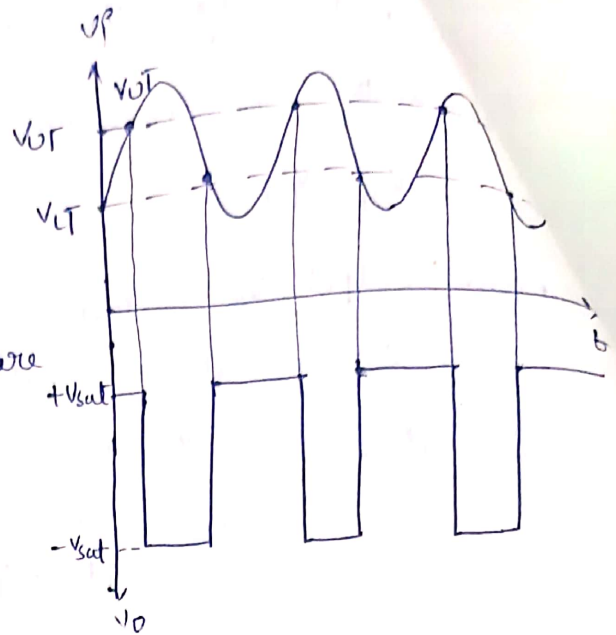


To get symmetrical square wave-

the reference voltage is set to '0' volts


and frequency  $f = 1/T$  and  $V_{UT} = V_m \sin \theta$

with shifted on phase angle of '0'.

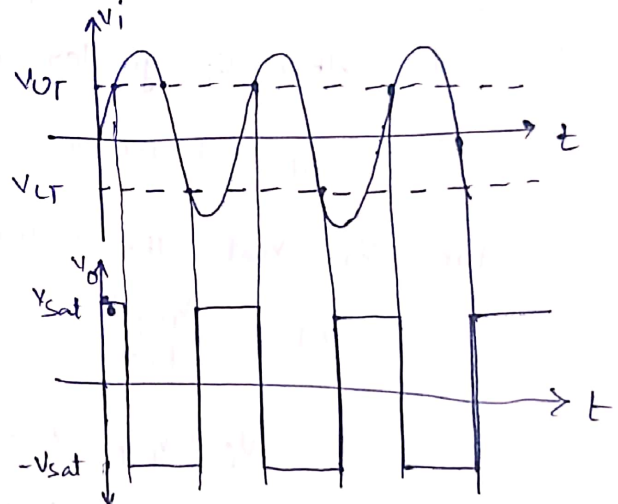

Application:-

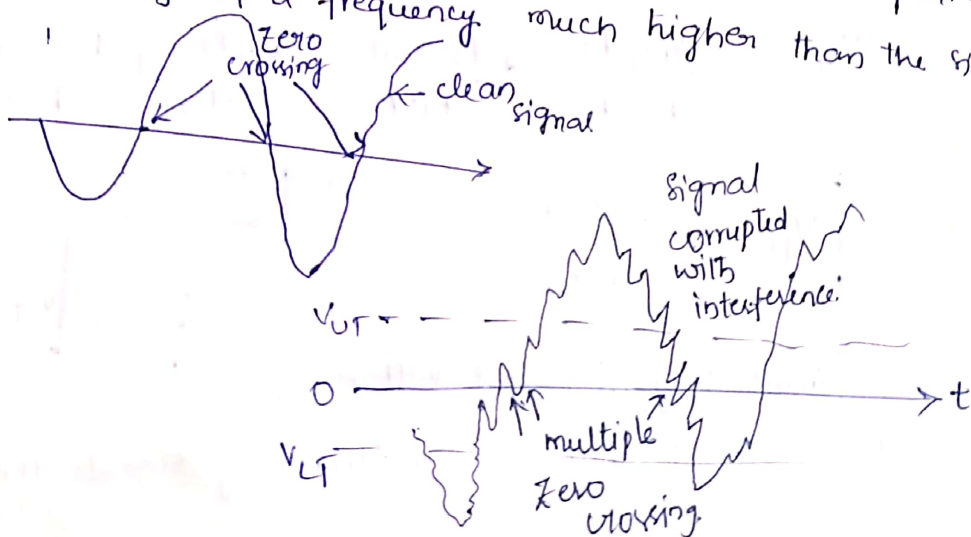→ The application of hysteresis is in the detection and counting of the zero crossing of an arbitrary waveform if it is superimposed with interference say of a frequency much higher than the signal.





Schmitt trigger circuit  $R_2 = 100\Omega$ ,  $R_1 = 50K\Omega$ ,  $V_{ref} = 0V$ ,  
 sine wave and saturation voltage  $= \pm 14V$ . Determine  
 voltage  $V_{UT}$  &  $V_{LT}$ .

$$V_{ref} = 0V.$$

$$V_{UT} = \frac{R_1 V_{ref}}{R_1 + R_2} + \frac{R_2 V_{sat}}{R_1 + R_2}$$

$$= 0 + \frac{100(+14)}{100 + 50K} \Rightarrow \boxed{V_{UT} = 27mV}$$

$$\boxed{V_{LT} = -27mV}$$

Since  $V_{UT} = -V_{LT}$  when  $V_{ref} = 0V$ .

Q) A Schmitt trigger with the upper threshold level  $V_{UT} = 0V$  and hysteresis width  $V_H = 0.2V$  converts a  $1kHz$  sine wave of amplitude  $4V_{p-p}$  into a square wave. Calculate the time duration of the negative and +ve portion of the o/p w/f  $q$ .

sol).

$$\text{Given } V_{UT} = 0V$$

$$V_{LT} = -0.2V$$

$$V_{UT} = V_m \sin \theta$$

$$V_{LT} = V_m \sin(180 + \theta)$$

$$-0.2 = -2 \sin \theta$$

$$\sin \theta = 0.1$$

$$\text{Time period } T = \frac{1}{f} = \frac{1}{10^3} = 1msec$$

$$\sin \theta = \frac{0.1}{2}$$

$$\sin \theta = 0.05$$

$$T_1 = 0.5 + 0.015$$

$$T_1 = 0.516ms$$

$$T_2 = 0.5 - 0.015$$

$$T_2 = 0.485msec$$

